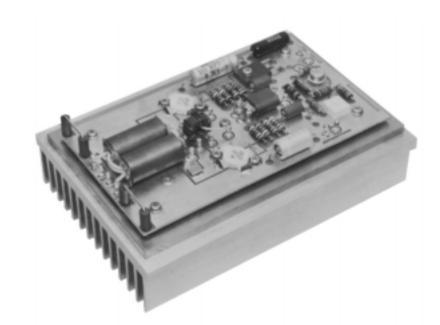


GET 300 WATTS PEP LINEAR ACROSS 2 TO 30 MHz FROM THIS PUSH-PULL AMPLIFIER

Prepared by: Helge Granberg Circuits Engineer, SSB

RCHIVE INFORMATION




(The heat sink shown with amplifier is sufficient only for short test periods under forced air cooling.)

This bulletin supplies sufficient information to build a push-pull linear amplifier for 300 watts of PEP or CW output power across the 2- to 30-MHz band. One of Motorola's new high-power transistors developed for single-sideband, MRF422, is used in this application.

Like all transistors in its family of devices, MRF422 combines single-chip construction that is advancing the state-of-the-art, and improved packaging to accommodate the low collector efficiencies encountered in class B operation. Rated maximum output power is 150 watts CW or PEP with intermodulation distortion spec'd at - 30 dB maximum, - 33 dB typical. Although not recommended, a saturated power level of 240- to 250-W is achievable. Maximum allowable dissipation is 300 W at 25°C.

Because of its excellent load and line voltage regulating capabilities, an integrated circuit bias regulator is used in the amplifier. The MPC1000, originally described in this bulletin, consisted of a MC1723 chip and a built-in pass transistor. The manufacture of this device has been discontinued however, and the board lay-out was modified to incorporate the above two in separate packages. The load regulation typically measures less than 2% at current levels up to 0.5 A, which assumes an h_{FE} of 40 for the RF power devices. The board surface provides a sufficient heat sink for the 2N5990 pass transistor, but a separate heat dissipator, such as Thermalloy 6107 can be added if necessary. With the component values shown, the bias is adjustable from 0.4 to 0.8 volts.

Gain flatness over the band is achieved using base input networks R_1C_2 and R_2C_3 and negative feedback through R_3 and R_4 . The networks represent a series reactance of 0.69 ohms at 30 MHz rising to 1.48 ohms at 2 MHz. A single-turn winding in the collector choke provides a low-impedance negative feedback source, thus R_3 and R_4 determine the amount. The reactance of C_4 reduces feedback at high frequencies with the result that feedback increases an average of 4 dB per octave at decreasing frequency.

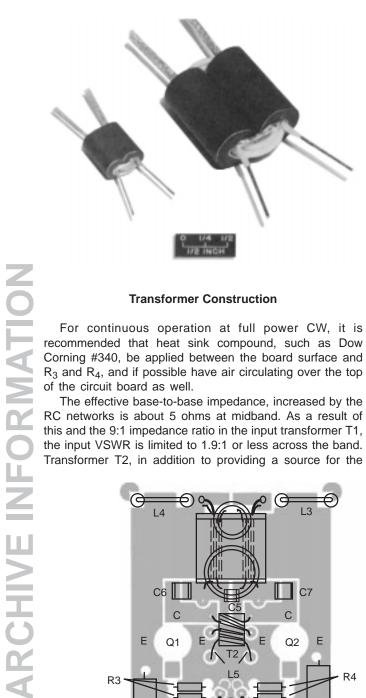

Transformer Construction

For continuous operation at full power CW, it is recommended that heat sink compound, such as Dow Corning #340, be applied between the board surface and R₃ and R₄, and if possible have air circulating over the top of the circuit board as well.

The effective base-to-base impedance, increased by the RC networks is about 5 ohms at midband. As a result of this and the 9:1 impedance ratio in the input transformer T1, the input VSWR is limited to 1.9:1 or less across the band. Transformer T2, in addition to providing a source for the feedback and carrying the dc collector current, acts as the rf center tap of the output transformer. To construct T2, wind 5 turns of 2 twisted pairs of AWG No. 22 enameled wire on a Stackpole 57-9322 toroid (Indiana General F627-8Q1).



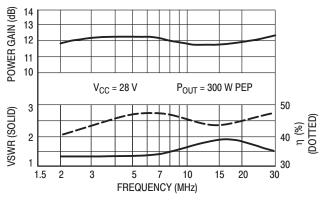


Figure 1. Collector Efficiency, Power Gain and VSWR vs Frequency

A Stackpole dual balun ferrite core 57-1845-24B is used for T1. The secondary is made of 1/8" copper braid, through which three turns of the primary winding (No. 22 Teflon[®] insulated hook-up wire) are threaded. The construction of T3 is similar to that of T1. It employs two Stackpole 57-3238* ferrite sleeves which are cemented together for easier construction. The primary is made of 1/4" copper braid, through which three turns of No. 16 Teflon® insulated wire are threaded for the secondary .

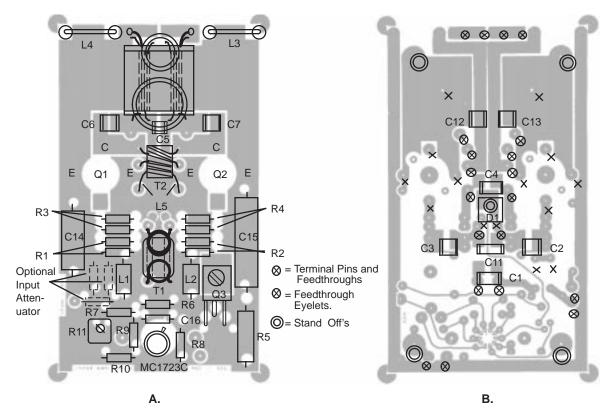

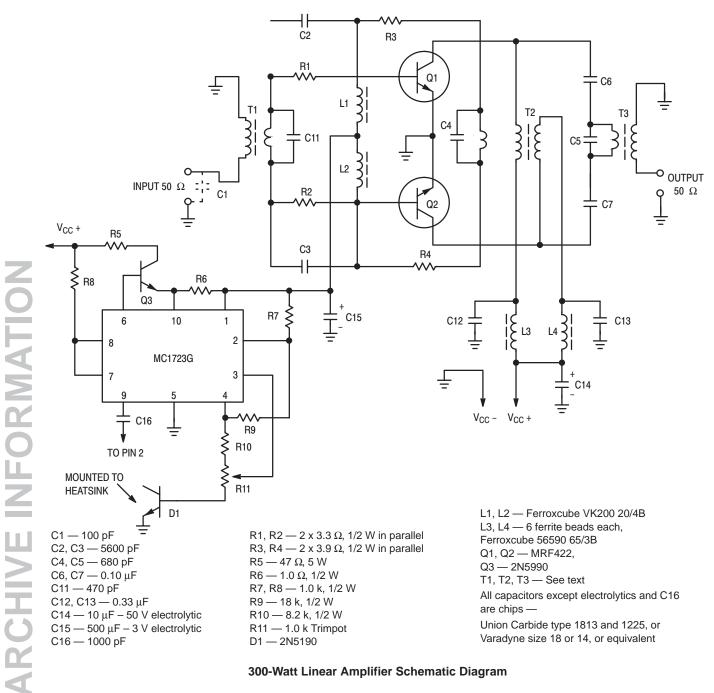

300-Watt Linear Amplifier Schematic Diagram

For production quantities, the braid in T₃ may be made of brass or copper tubes with their ends soldered to pieces of PC board laminate. See cover picture and Motorola AN-749 for details.

The bandwidth characteristics of these transformers do not equal those of the transmission line type, but they're much easier to duplicate.

The measured performance of the amplifier is shown in figures 1, 2, and 3 and harmonic rejection data in table 1.

Table 1. Output Harmonic Contents, Measured at 300-W CW


(all test data taken using a tuned output, narrow band signal source).

	2nd	3rd	4th	5th
f (Mhz)	(dB below the carrier)			
30.0	- 38	- 25	- 34	- 48
20.0	- 33	- 13	- 43	- 45
15.0	- 50	- 10	- 51	- 47
7.5	- 40	- 30	- 55	- 47
4.0	- 37	- 22	- 55	- 37
2.0	- 36	- 18	- 45	- 37

^{*} A similar product is available from Fair-Rite Products Corp., Wallkill, N.Y.,12589

[®] Registered trademark of DuPont

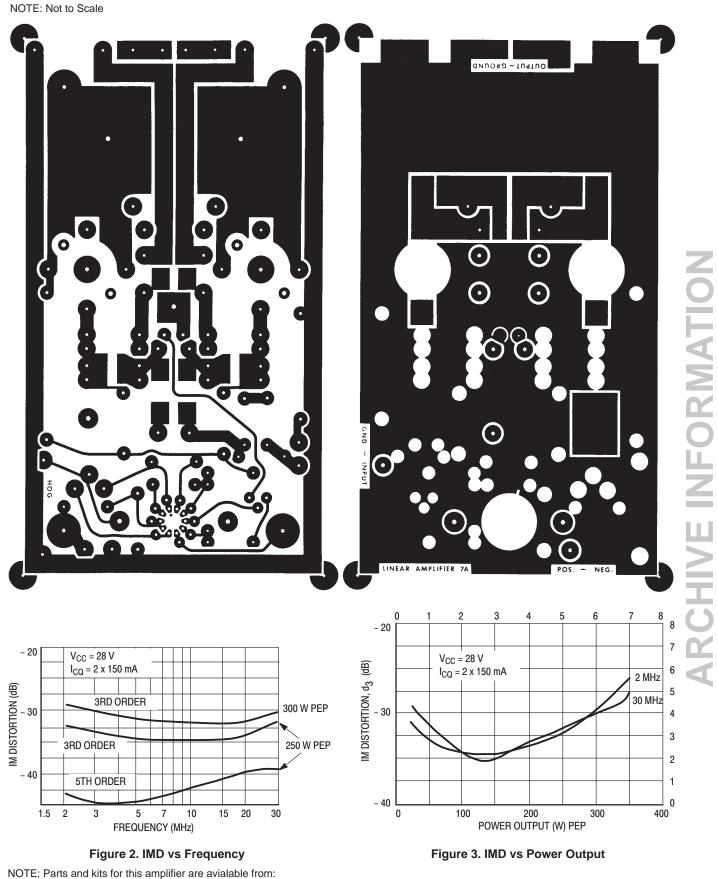PCB, chips capacitors, transformers T₁, T₂, T₃, and ferrite beads are available from: COMMUNICATIONS CONCEPTS, 2648 N. Aragon Ave., Kettering, Ohio 45420. Telephone: (513) 294-8425.



RF Application Reports

Z

EB27A

Communication Concepts, Inc.

Beavercreek, Ohio 45434-5840

508 Millstone Drive

(513) 426-8600

Motorola reserves the right to make changes without further notice to any products herein. Motorola makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does Motorola assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation consequential or incidental damages. "Typical" parameters can and do vary in different applications. All operating parameters, including "Typicals" must be validated for each customer applications by customer's technical experts. Motorola are not does Motorola are not designed, intended, or authorized for use as components in systems intended for surgical implant into the body, or other applications intended to support or sustain life, or for any other application in which the failure of the Motorola product could create a situation where personal injury or death may occur. Should Buyer purchase or use Motorola products or any such applications, Buyer shall indemnify and hold Motorola and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death may occur. Should was negligent regarding the design or manufacture of the part. Motorola and (A) are registered trademarks of Motoroia, Inc. Motorola may Bud Motorola was negligent regarding the design or manufacture of the part.

Literature Distribution Centers:

USA: Motorola Literature Distribution; P.O. Box 20912; Phoenix, Arizona 85036.

EUROPE: Motorola Ltd.; European Literature Centre; 88 Tanners Drive, Blakelands, Milton Keynes, MK14 5BP, England.

JAPAN: Nippon Motorola Ltd.; 4-32-1, Nishi-Gotanda, Shinagawa-ku, Tokyo 141, Japan.

ASIA PACIFIC: Motorola Semiconductors H.K. Ltd.; Silicon Harbour Center, No. 2 Dai King Street, Tai Po Industrial Estate, Tai Po, N.T., Hong Kong.



ARCHIVE INFORMATIC